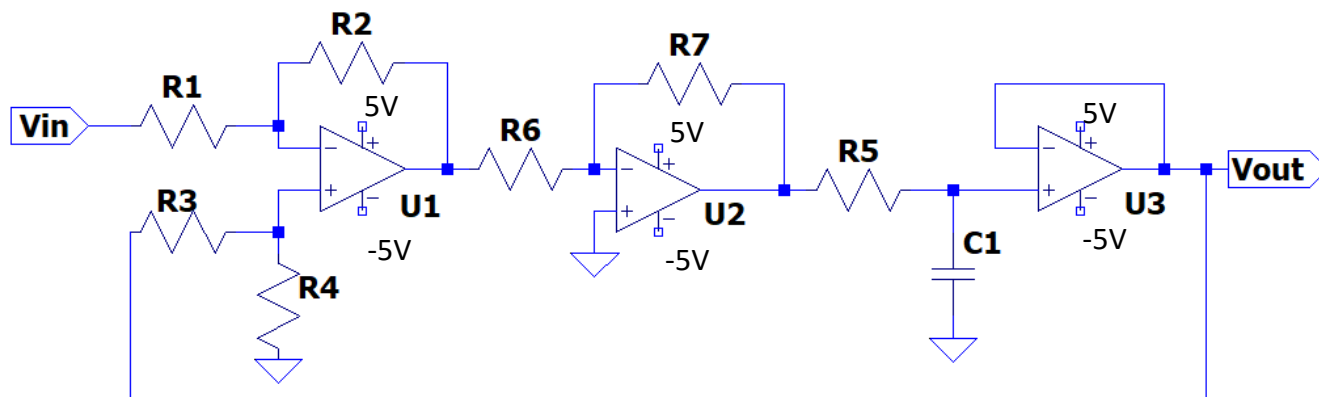


REPORT

Experiment 1: RC circuit with unit feedback




	rise time (s)	delay time (s)	steady-state error (V)
Theoretical Result			0.5
Experiment Result	0.285	0.080	0.530
Simulation Result	0.2197	0.0737	0.5000

注意事項:請參考投影片第 5 頁的定義

1. Calculate the closed loop transfer function.

$$\begin{aligned}
 V_{out} &= -1 \times (V_{out} - V_{in}) \times \frac{1}{0.2s + 1} \\
 \Rightarrow (0.2s + 1)V_{out} &= -V_{out} + V_{in} \\
 \Rightarrow (0.2s + 2)V_{out} &= V_{in} \\
 \Rightarrow \frac{V_{out}}{V_{in}} &= \frac{1}{0.2s + 2} \#
 \end{aligned}$$

2. V_{out} and V_{in} waveform (1 pic):

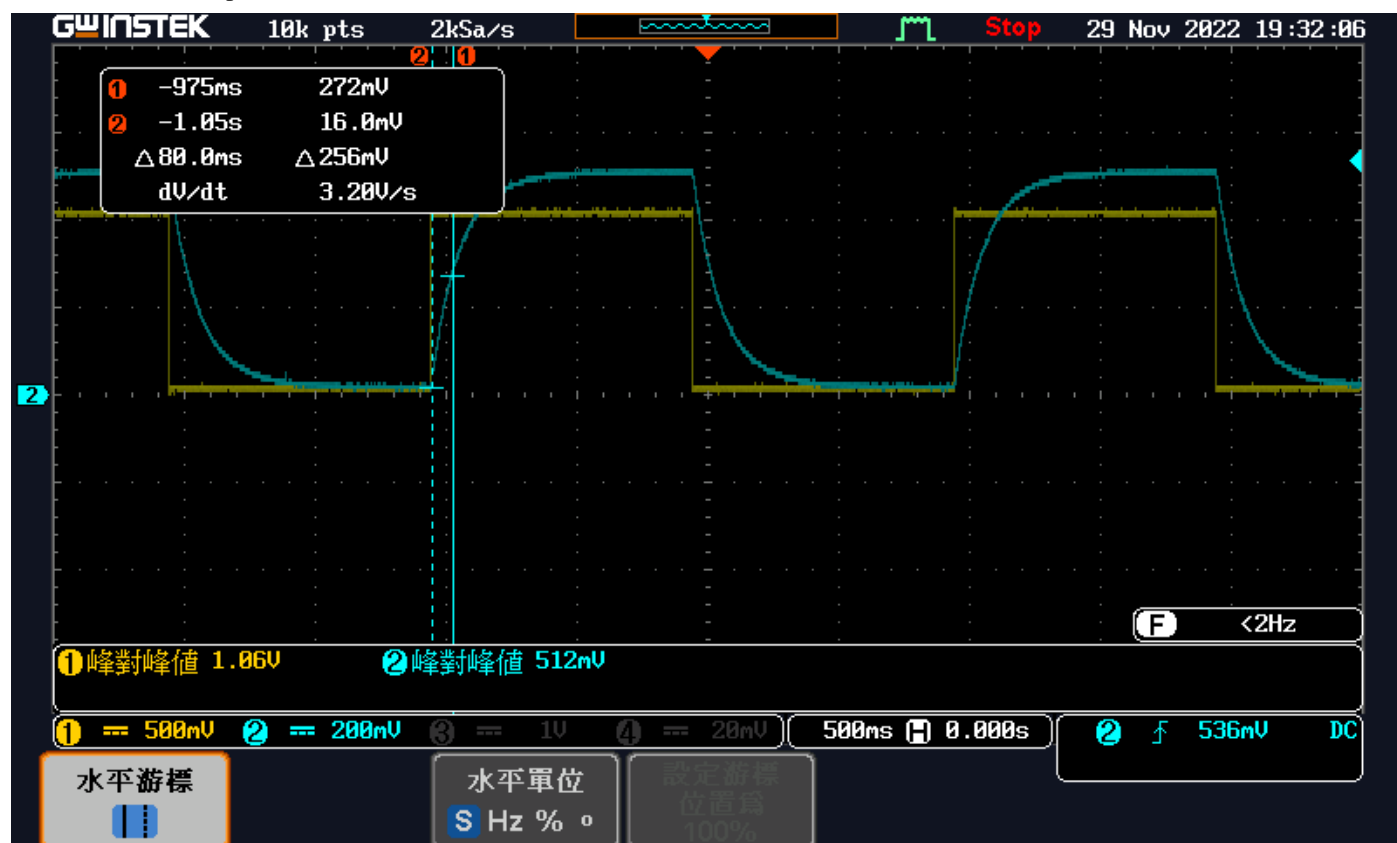


3. Simulation

Closed loop transfer function from command window:

$$\text{sys} = \frac{1}{0.2 s + 2}$$

The unit step response(1 pic):

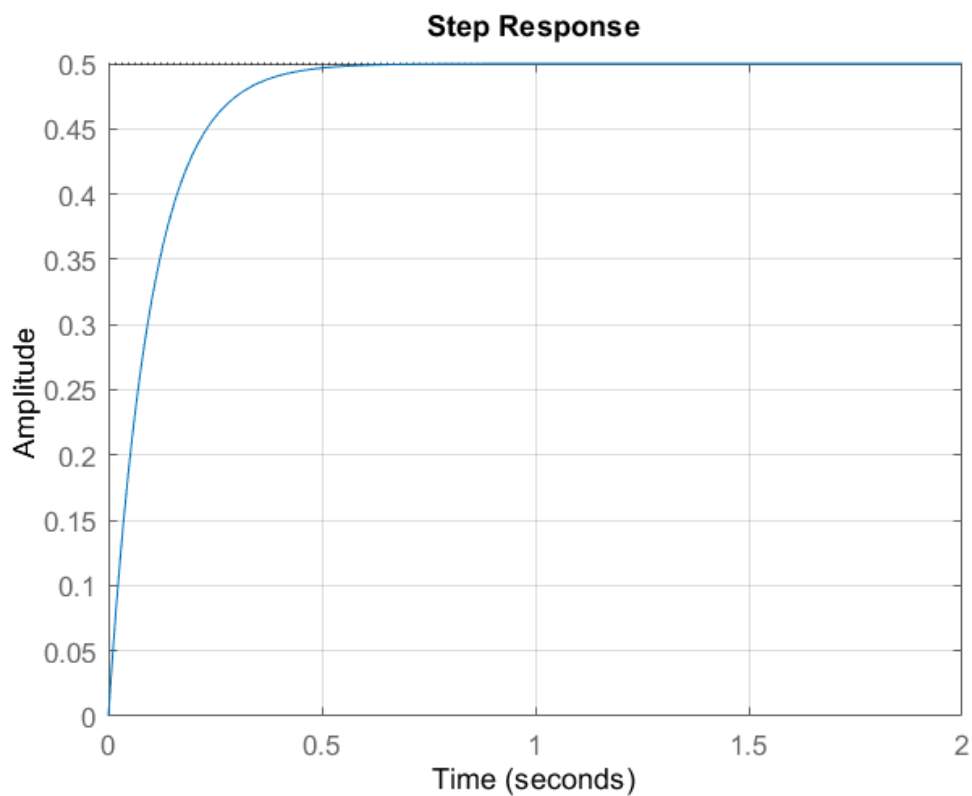

ans =

struct with fields:

```
RiseTime: 0.2197
SettlingTime: 0.3912
SettlingMin: 0.4523
SettlingMax: 0.5000
Overshoot: 0
Undershoot: 0
Peak: 0.5000
PeakTime: 1.0546
```


delayTime =

0.0737

sserror =

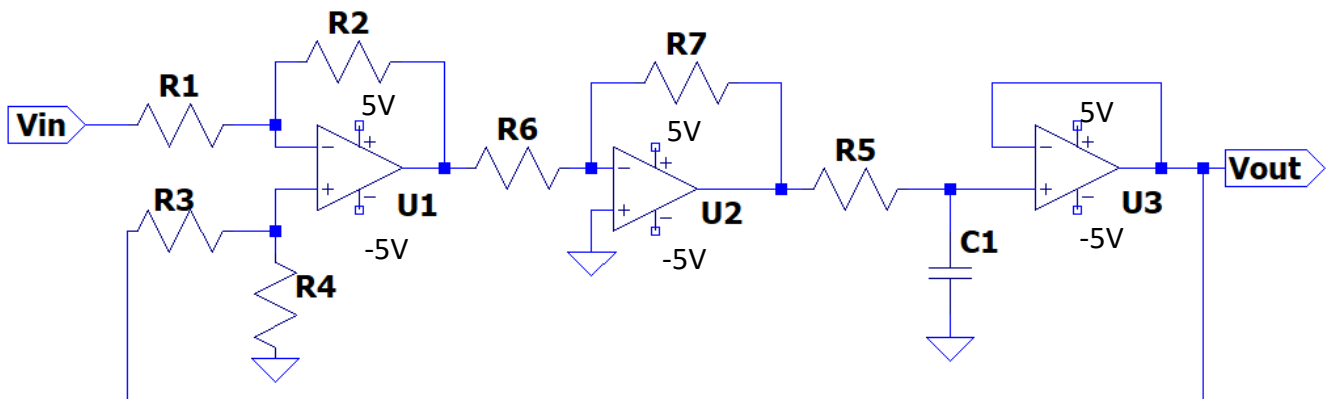0.5000

Experiment 2: RC circuit with P-controller and unit feedback



	rise time (s)	delay time (s)	steady-state error (V)
Theoretical Result			0.0909
Experiment Result	0.050	0.014	0.1
Simulation Result	0.0399	0.0134	0.0909

注意事項:請參考投影片第 5 頁的定義

1. Calculate K_p and the closed loop transfer function.

Assume V_2 is the output of U1. The relation of input and output of difference amplifier:

$$V_2 = V_{out} - V_{in}$$

Assume V_3 is the output of U2. The relation of input and output of inverting amplifier:

$$\begin{aligned} \frac{0 - V_2}{R_6} + \frac{0 - V_3}{R_7} &= 0 \\ \Rightarrow V_3 &= -\frac{R_7}{R_6} V_2 \end{aligned}$$


Substitute $V_2 = V_{out} - V_{in}$:

$$\begin{aligned} &= \frac{100}{10} (V_{in} - V_{out}) \\ &= 10(V_{in} - V_{out}) \end{aligned}$$

The relation of input and output of plant:

$$\begin{aligned} 10V_{in} - 10V_{out} &= (sR_5C_1 + 1)V_{out} \\ \Rightarrow V_{out} &= \frac{10V_{in}}{sR_5C_1 + 11} \\ \Rightarrow K_p &= 10_{\#} \\ \Rightarrow V_{out} &= \frac{10}{0.2s + 11} V_{in}_{\#} \end{aligned}$$

2. V_{out} and V_{in} waveform (1 pic):

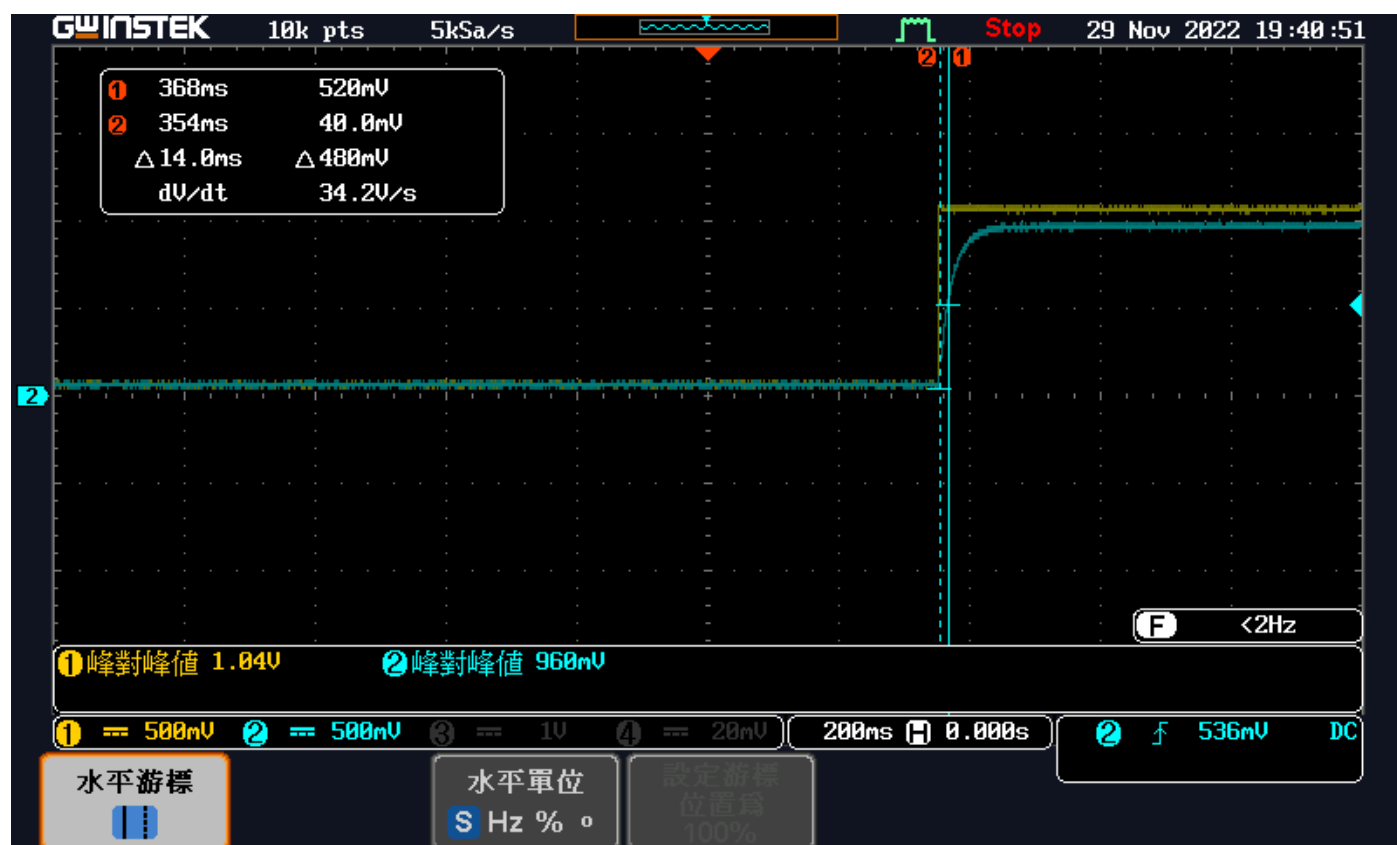


3. Simulation

Closed loop transfer function from command window:

$$\text{sys} = \frac{10}{0.2 s + 11}$$

The unit step response(1 pic):

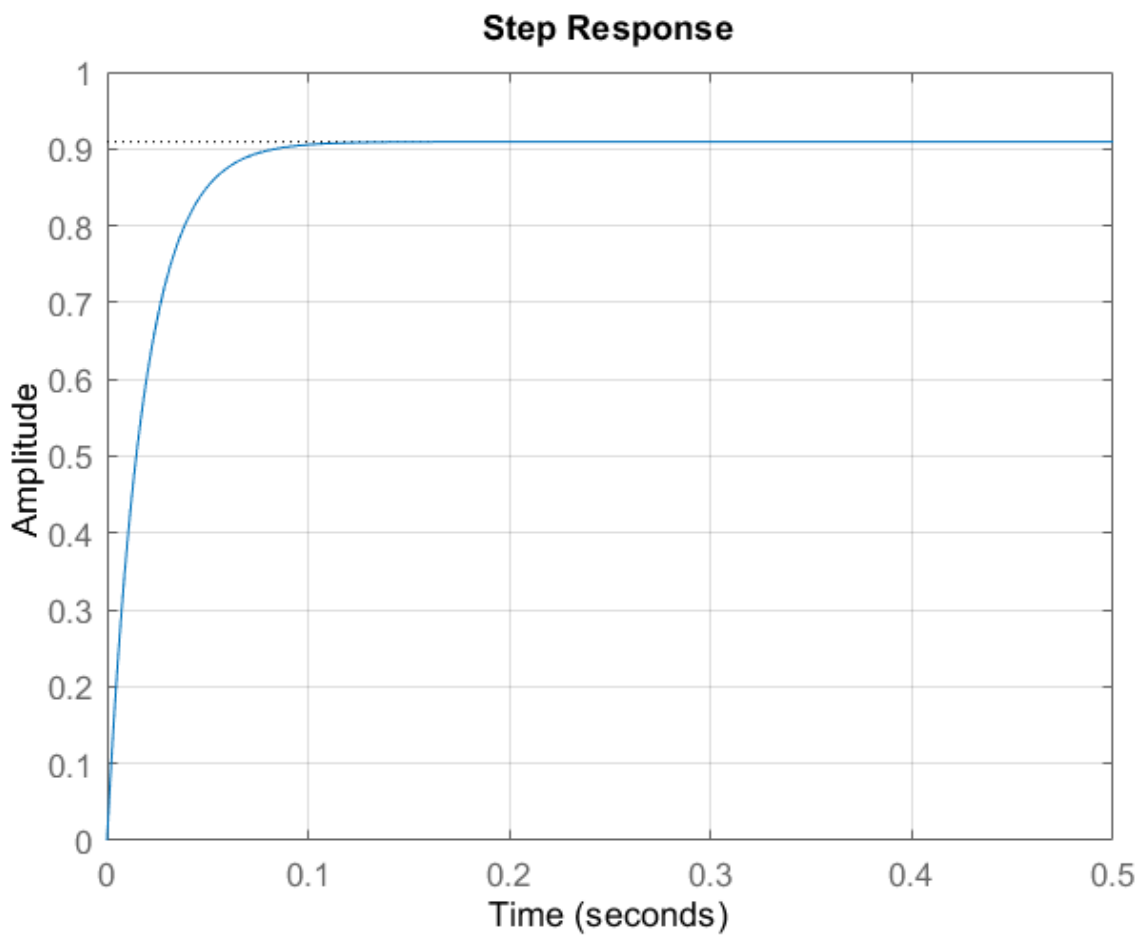

ans =

struct with fields:

RiseTime: 0.0399
SettlingTime: 0.0711
SettlingMin: 0.8223
SettlingMax: 0.9091
Overshoot: 0
Undershoot: 0

Peak: 0.9091

PeakTime: 0.1917

delayTime =

0.0134

sserror =


0.0909

Discuss:

Try to explain the effect of the gain K_P on the overall system.

Make the response faster and improve the steady state error.

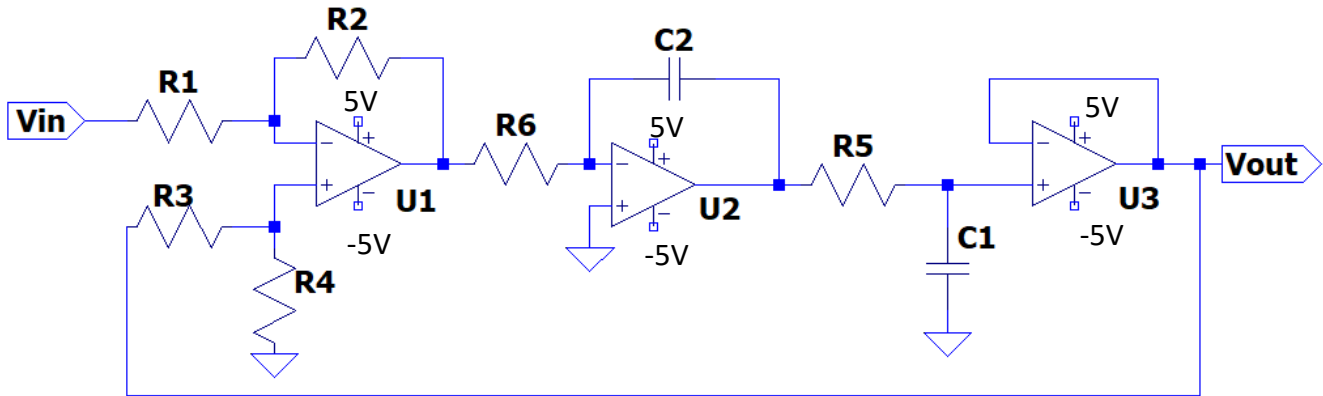Experiment 3: RC circuit with I-controller and unit feedback



	Maximum overshoot (%)	peak time (s)	rise time (s)	delay time (s)	settling time for 5% (s)	steady-state error (V)
Theoretical Result						0
Experiment Result	52.83	0.150	0.092	0.055	1.31	0.010
Simulation Result	70.2118	0.1405	0.0509	0.2817	1.5630	0.0064

注意事項:請參考投影片第 7 頁的定義

1. Calculate K_I and the closed loop transfer function.

The output of U1 V_1 is equal to

$$V_1 = V_{out} - V_{in}$$

The relationship between V_1 and V_2 around U2 is

$$\frac{0 - V_1}{R_6} + \frac{0 - V_2}{\frac{1}{sC_2}} = 0$$

Substitute $V_1 = V_{out} - V_{in}$:

$$\begin{aligned} \Rightarrow V_2 &= \frac{1}{sC_2R_6}(V_{in} - V_{out}) \\ &= \frac{1}{0.01s}(V_{in} - V_{out}) \\ \Rightarrow K_I &= 100_{\#} \end{aligned}$$

The relationship between V_2 and V_{out} :

$$\begin{aligned} \frac{V_{out} - V_2}{R_5} + \frac{V_{out}}{\frac{1}{sC_1}} &= 0 \\ \Rightarrow V_{out} - V_2 &= -sC_1R_5V_{out} \end{aligned}$$


Substitute V_2 :

$$\begin{aligned} \Rightarrow (sC_1R_5 + 1)V_{out} &= V_2 = \frac{1}{0.01s}(V_{in} - V_{out}) \\ \Rightarrow (0.2s + 1)(0.01s)V_{out} + V_{out} &= V_{in} \end{aligned}$$

$$\Rightarrow \left(\frac{1}{500} s^2 + \frac{1}{100} s + 1 \right) V_{out} = V_{in}$$

$$\Rightarrow V_{out} = \frac{1}{0.002s^2 + 0.01s + 1} V_{in} \#$$

2. V_{out} and V_{in} waveform (1 pic):

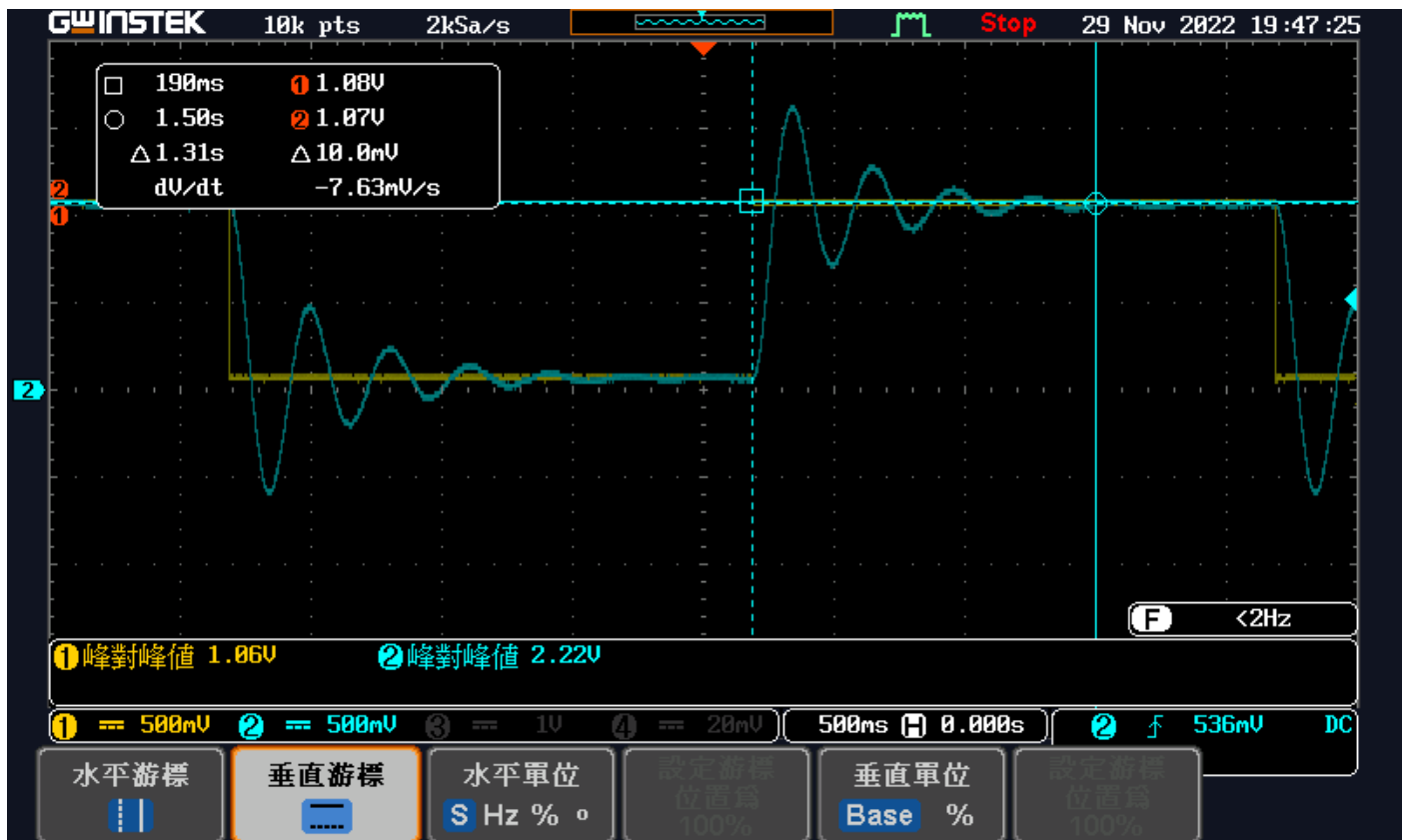


3. Simulation

Closed loop transfer function from command window:

$$\text{sys} = \frac{1}{0.002 s^2 + 0.01 s + 1}$$

The unit step response(1 pic):

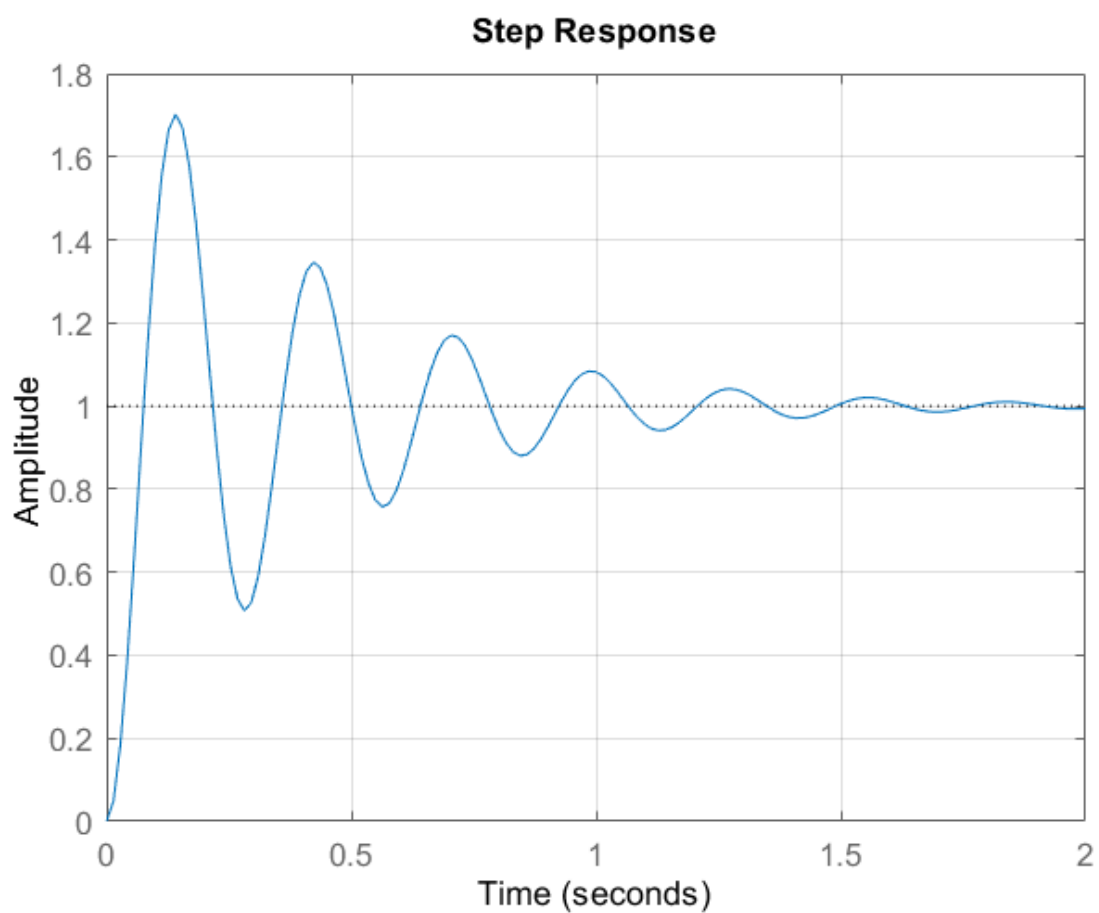

ans =

struct with fields:

```
RiseTime: 0.0509
SettlingTime: 1.5630
SettlingMin: 0.5072
SettlingMax: 1.7021
Overshoot: 70.2118
Undershoot: 0
```

Peak: 1.7021

PeakTime: 0.1405

delayTime =

0.2817

sserror =

0.0064

Discuss:


Try to explain why the steady-state error is close to zero and the effect of the gain K_I on the overall system.

When the output reach steady state, capacitor C2 will be open circuit because the current through it

$\frac{V_{out}-V_{in}-0}{R_6}$ is approximately 0. Therefore, the steady state error is close to zero.

The effect of the gain K_I is to eliminate the steady state error.

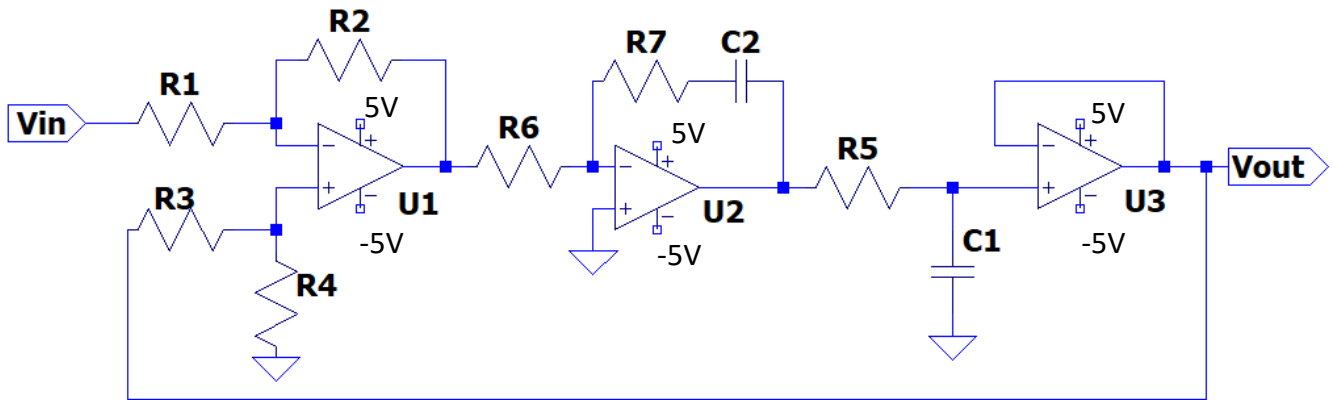Experiment 4: RC circuit with PI-controller and unit feedback



	Maximum overshoot (%)	peak time (s)	rise time (s)	delay time (s)	settling time for 5% (s)	steady-state error (V)
Theoretical Result						0
Experiment Result	3.774	0.085	0.070	0.019	0.198	0.004
Simulation Result	4.8838	0.0974	0.0358	0.0127	0.2007	0.00064794

注意事項:請參考投影片第 7 頁的定義

1. Calculate K_p , K_I and the closed loop transfer function.

The difference amplifier:

$$V_1 = V_{out} - V_{in}$$


The PI controller:

$$\begin{aligned}
 \frac{0 - V_1}{R_6} + \frac{0 - V_2}{R_7 + \frac{1}{sC_2}} &= 0 \\
 \Rightarrow \frac{V_2}{\frac{sC_2R_7 + 1}{sC_2}} &= -\frac{V_1}{R_6} \\
 \Rightarrow V_2 &= -\frac{1}{R_6} \times \frac{sC_2R_7 + 1}{sC_2} V_1 \\
 &= -\frac{C_2R_7s + 1}{sC_2R_6} V_1 \\
 &= \frac{\frac{s}{10} + 1}{\frac{s}{100}} (V_{in} - V_{out}) \\
 &= \frac{10s + 100}{s} (V_{in} - V_{out}) \\
 \Rightarrow K_p &= 10, K_I = 100_{\#}
 \end{aligned}$$

The plant:

$$\begin{aligned}
 \frac{V_{out}}{\frac{1}{sC_1}} + \frac{V_{out} - V_2}{R_5} &= 0 \\
 \Rightarrow (sC_1R_5 + 1)V_{out} &= V_2 \\
 \Rightarrow V_{out} &= \frac{1}{sC_1R_5 + 1} V_2 \\
 &= \frac{1}{0.2s + 1} \left(\frac{10s + 100}{s} \right) (V_{in} - V_{out}) \\
 &= \frac{10s + 100}{0.2s^2 + s} (V_{in} - V_{out}) \\
 \Rightarrow V_{out} &= \frac{\frac{10s + 100}{0.2s^2 + s}}{1 + \frac{10s + 100}{0.2s^2 + s}} V_{in} \\
 \Rightarrow V_{out} &= \frac{10s + 100}{0.2s^2 + 11s + 100} V_{in} \quad \#
 \end{aligned}$$

2. V_{out} and V_{in} waveform (1 pic):

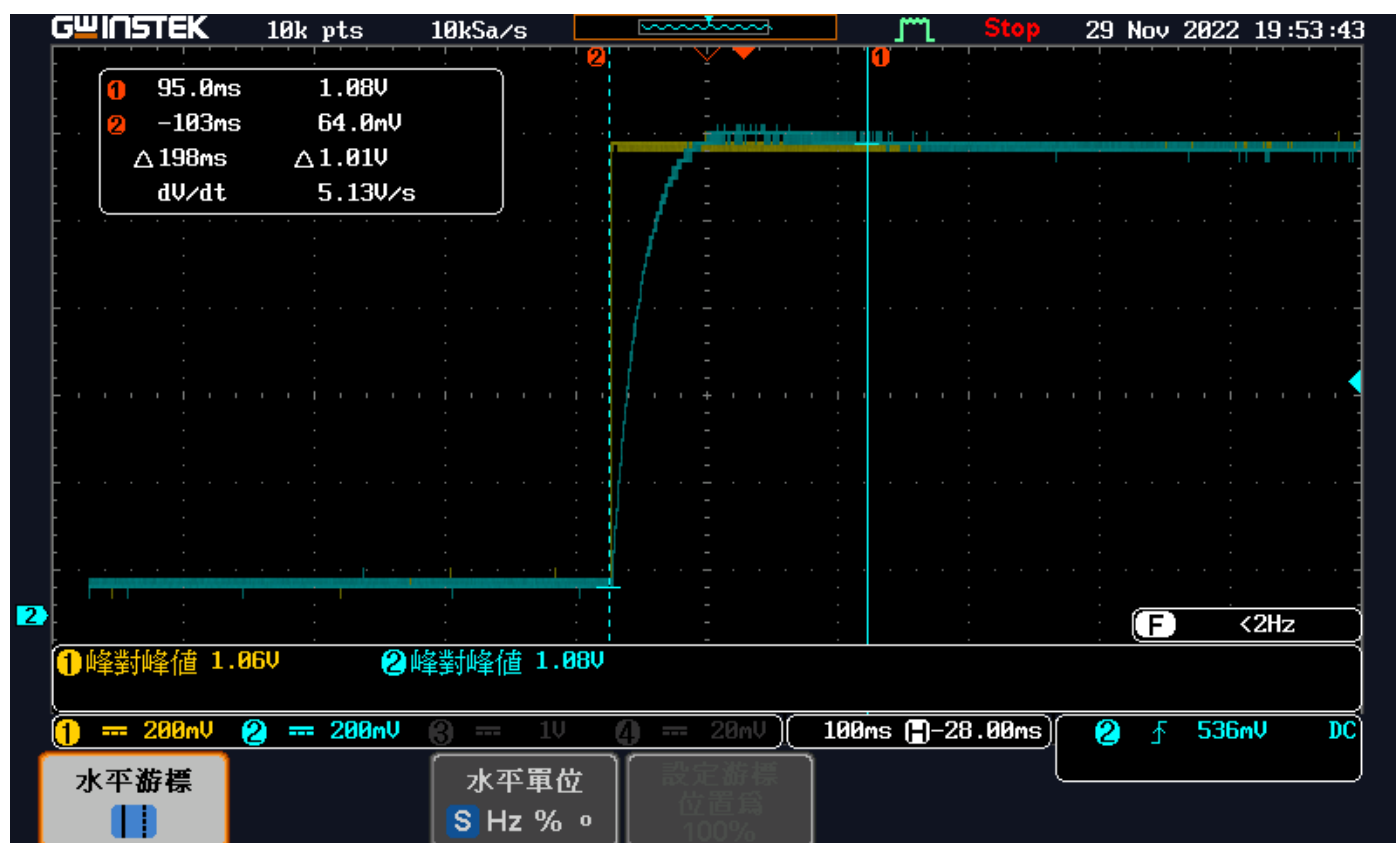


3. Simulation

Closed loop transfer function from command window:

sys =

$$\frac{0.1 s + 1}{0.002 s^2 + 0.11 s + 1}$$

The unit step response(1 pic):

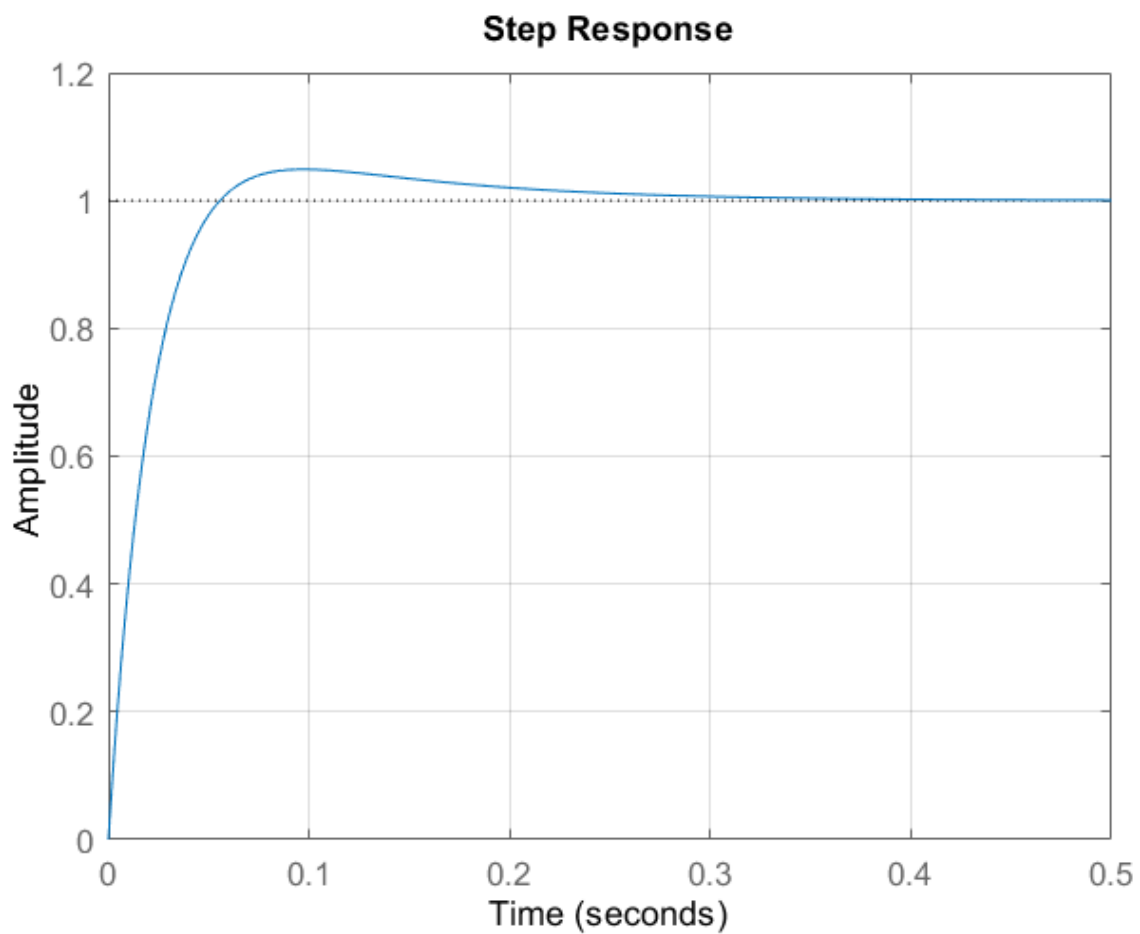

ans =

struct with fields:

```
RiseTime: 0.0358
SettlingTime: 0.2007
SettlingMin: 0.9017
SettlingMax: 1.0488
Overshoot: 4.8838
Undershoot: 0
```

Peak: 1.0488

PeakTime: 0.0974

delayTime =

0.0127

sserror =

6.4794e-04

Discuss:

Try to explain the effect of PI-controller on the overall system and how to design K_p and K_I .

The PI-controller both the rise time and the steady state errors of the system.

Increasing K_p results in a faster response of the control system. However, an increase in K_p above a certain value can make the system unstable.

Increasing K_i helps in eliminating steady-state error, but increases oscillations and overshoot.