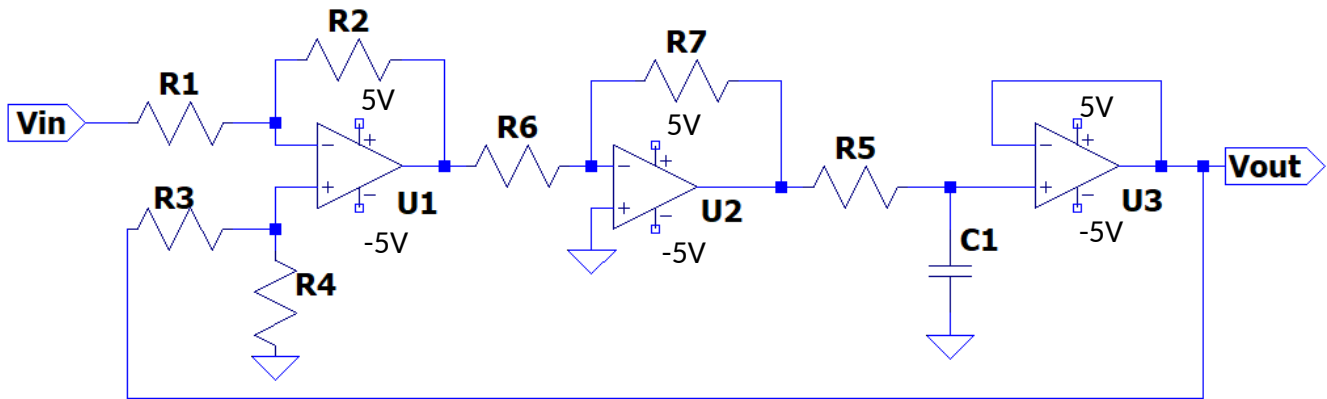


# REPORT

## Experiment 1: RC circuit with unit feedback



|                           | rise time<br>(s) | delay time<br>(s) | steady-state error<br>(V) |
|---------------------------|------------------|-------------------|---------------------------|
| <b>Theoretical Result</b> |                  |                   | <b>0.5</b>                |
| <b>Experiment Result</b>  | <b>0.285</b>     | <b>0.080</b>      | <b>0.530</b>              |
| <b>Simulation Result</b>  | <b>0.2197</b>    | <b>0.0737</b>     | <b>0.5000</b>             |

注意事項:請參考投影片第5頁的定義

1. Calculate the **closed loop transfer function**.


$$V_{out} = -1 \times (V_{out} - V_i) \times \frac{1}{0.2s+1}$$

$$\Rightarrow (0.2s+1)V_{out} = -V_{out} + V_i$$

$$\Rightarrow (0.2s+2)V_{out} = V_i$$

$$\Rightarrow \frac{V_{out}}{V_i} = \frac{1}{0.2s+2}$$

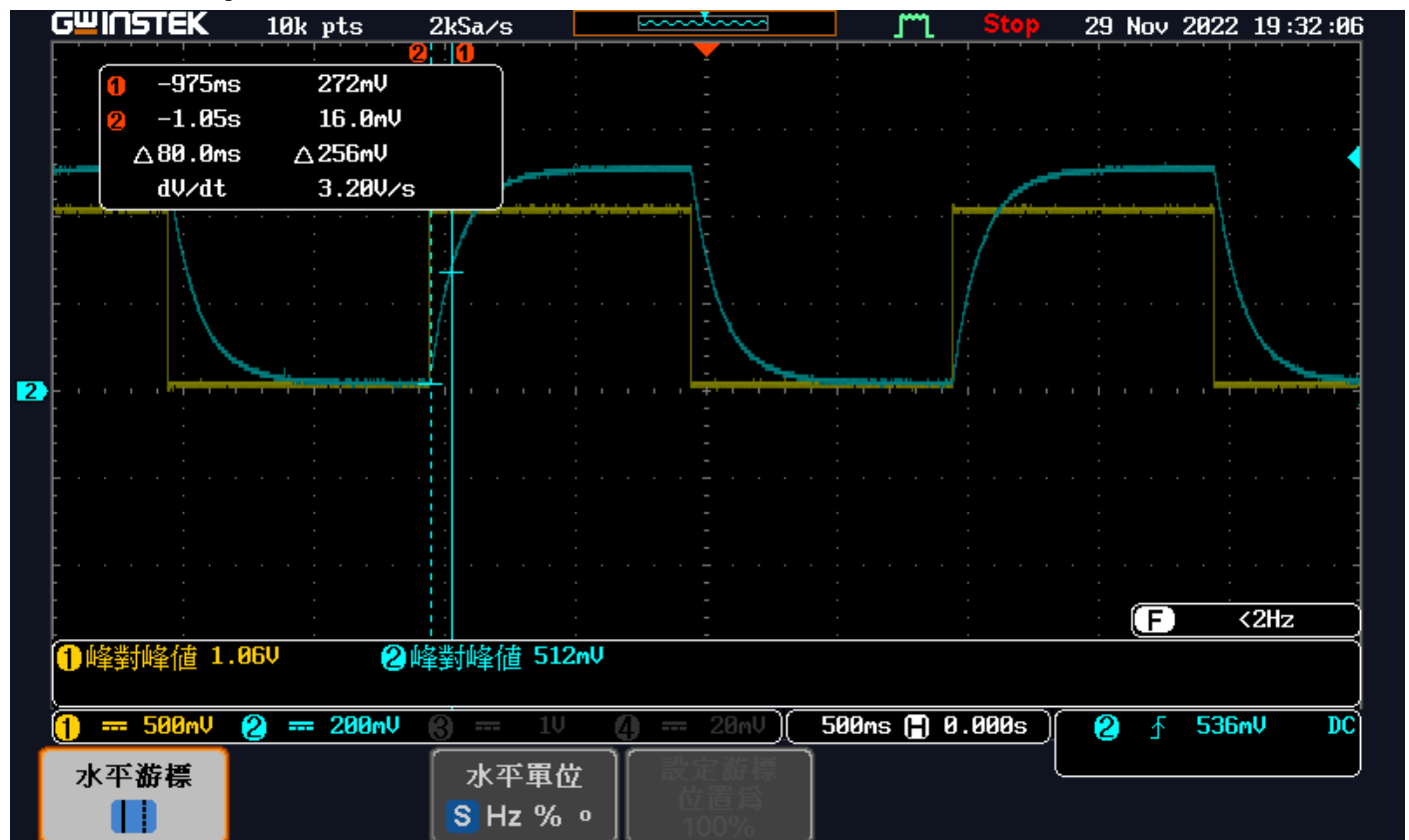2.  $V_{out}$  and  $V_{in}$  waveform (1 pic):




### 3. Simulation

Closed loop transfer function from command window:

$$\text{sys} = \frac{1}{0.2 s + 2}$$

The unit step response(1 pic):

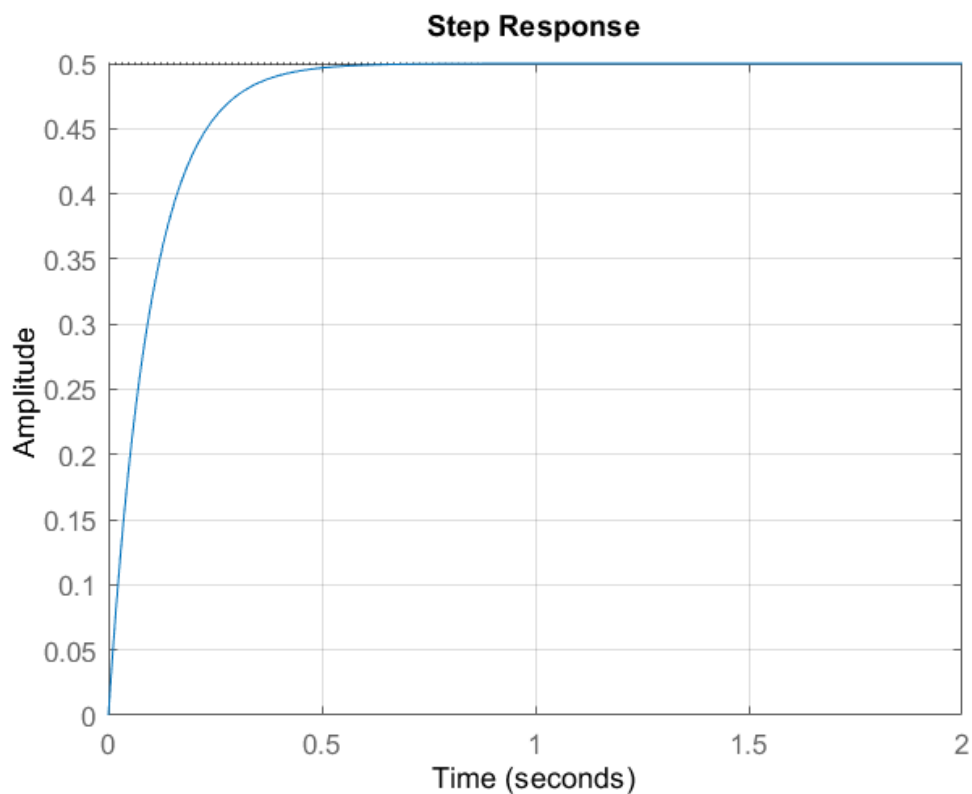

ans =

struct with fields:

```
RiseTime: 0.2197
SettlingTime: 0.3912
SettlingMin: 0.4523
SettlingMax: 0.5000
Overshoot: 0
Undershoot: 0
Peak: 0.5000
PeakTime: 1.0546
```


delayTime =

0.0737

sserror =

0.5000
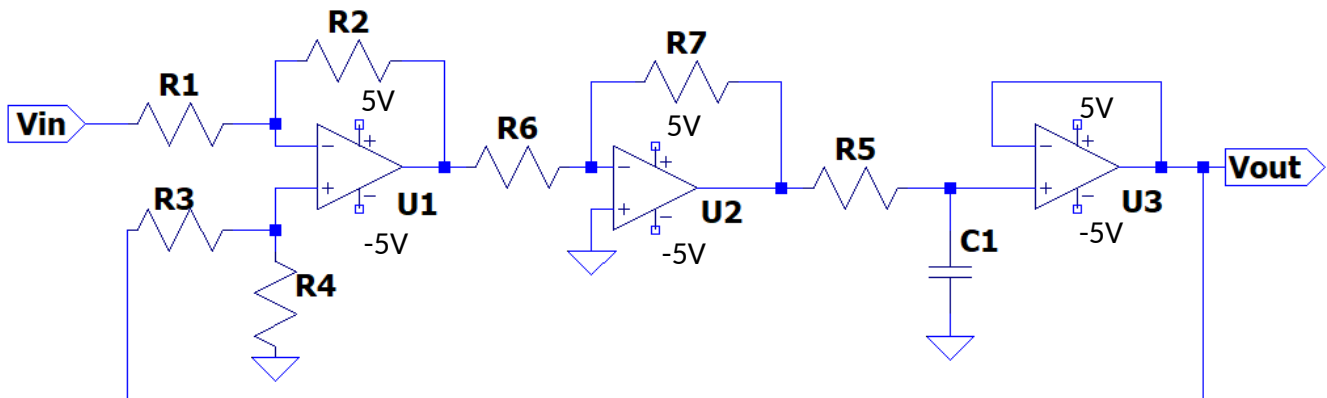
## Experiment 2: RC circuit with P-controller and unit feedback



|                           | rise time<br>(s) | delay time<br>(s) | steady-state error<br>(V) |
|---------------------------|------------------|-------------------|---------------------------|
| <b>Theoretical Result</b> |                  |                   | <b>0.0909</b>             |
| <b>Experiment Result</b>  | <b>0.050</b>     | <b>0.014</b>      | <b>0.1</b>                |
| <b>Simulation Result</b>  | <b>0.0399</b>    | <b>0.0134</b>     | <b>0.0909</b>             |

注意事項:請參考投影片第5頁的定義

1. Calculate  $K_p$  and the **closed loop transfer function**.

Assume  $V_2$  is the output of U1. The relation of input and output of difference amplifier:

$$V_2 = V_{out} - V_i$$

Assume  $V_3$  is the output of U2. The relation of input and output of inverting amplifier:

$$\frac{0 - V_2}{R_6} + \frac{0 - V_3}{R_7} = 0$$

$$\Rightarrow V_3 = \frac{-R_7}{R_6} V_2$$

Substitute  $V_2 = V_{out} - V_i$ :

$$i \frac{100}{10} (V_i - V_{out})$$

$$i 10 (V_i - V_{out})$$

The relation of input and output of plant:


$$10 V_i - 10 V_{out} = (s R_5 C_1 + 1) V_{out}$$

$$\Rightarrow V_{out} = \frac{10 V_i}{s R_5 C_1 + 11}$$

$$\Rightarrow K_p = 10_{\#}$$

$$\Rightarrow V_{out} = \frac{10}{0.2s + 11} V_i_{\#}$$

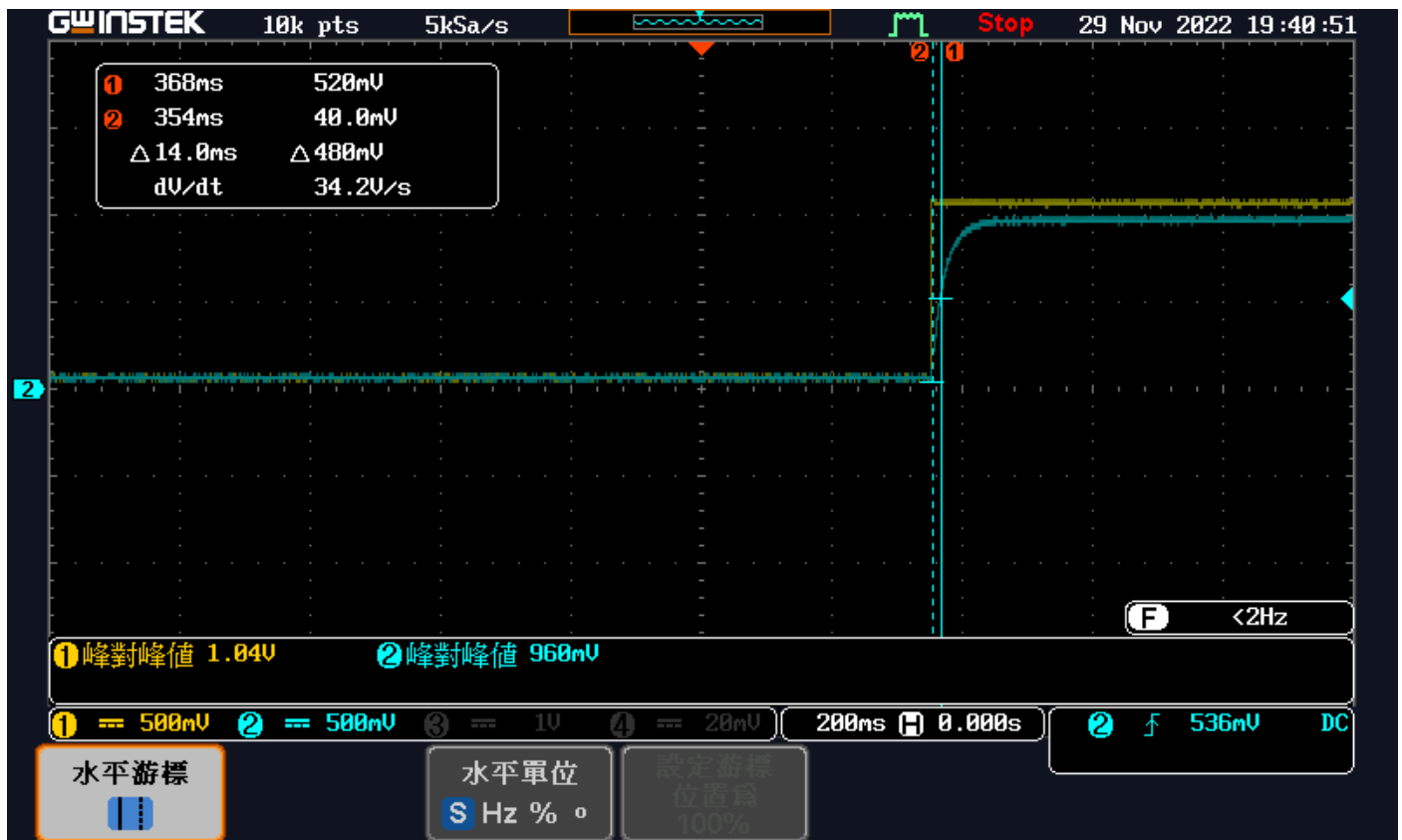2.  $V_{out}$  and  $V_{in}$  waveform (1 pic):




### 3. Simulation

Closed loop transfer function from command window:

$$\text{sys} = \frac{10}{0.2 s + 11}$$

The unit step response(1 pic):

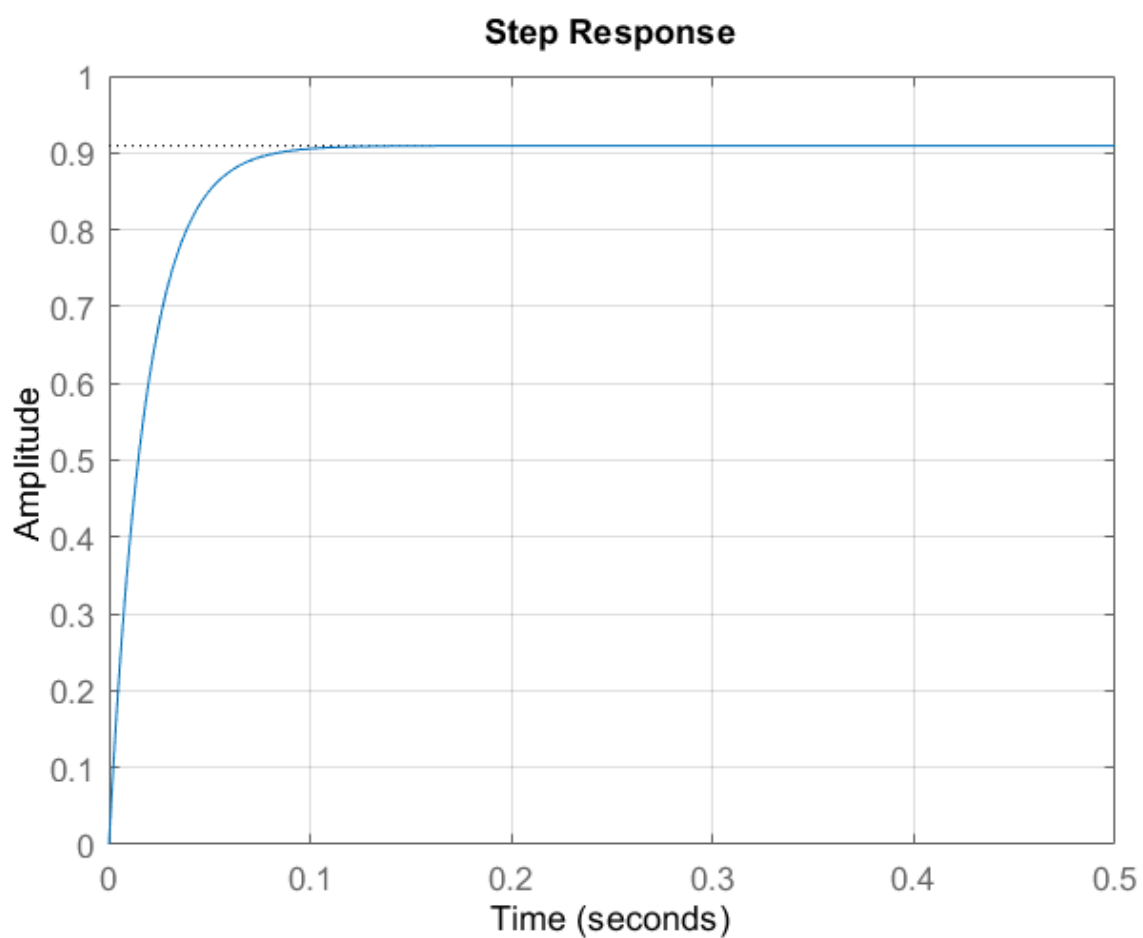

ans =

struct with fields:

```
RiseTime: 0.0399
SettlingTime: 0.0711
SettlingMin: 0.8223
SettlingMax: 0.9091
Overshoot: 0
Undershoot: 0
```

Peak: 0.9091  
PeakTime: 0.1917

delayTime =

0.0134

sserror =

0.0909


**Discuss:**

Try to explain the effect of the gain  $K_p$  on the overall system.

Make the response faster and improve the steady state error.


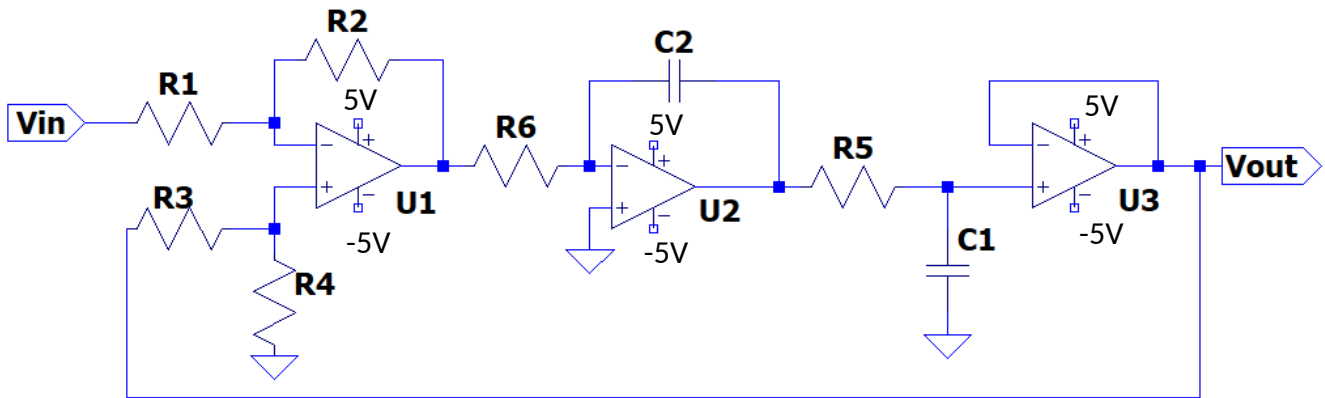
### Experiment 3: RC circuit with I-controller and unit feedback



|                    | Maximum overshoot (%) | peak time (s) | rise time (s) | delay time (s) | settling time for 5% (s) | steady-state error (V) |
|--------------------|-----------------------|---------------|---------------|----------------|--------------------------|------------------------|
| Theoretical Result |                       |               |               |                |                          | 0                      |
| Experiment Result  | 52.83                 | 0.150         | 0.092         | 0.055          | 1.31                     | 0.010                  |
| Simulation Result  | 70.2118               | 0.1405        | 0.0509        | 0.2817         | 1.5630                   | 0.0064                 |

注意事項:請參考投影片第7頁的定義

1. Calculate  $K_I$  and the **closed loop transfer function**.

The output of U1  $V_1$  is equal to

$$V_1 = V_{out} - V_i$$

The relationship between  $V_1$  and  $V_2$  around U2 is

$$\frac{0 - V_1}{R_6} + \frac{0 - V_2}{\frac{1}{sC_2}} = 0$$

Substitute  $V_1 = V_{out} - V_i$ :

$$\Rightarrow V_2 = \frac{1}{sC_2 R_6} (V_i - V_{out})$$

$$i \frac{1}{0.01 s} (V_i - V_{out})$$

$$\Rightarrow K_I = 100_{\#}$$

The relationship between  $V_2$  and  $V_{out}$ :

$$\frac{V_{out} - V_2}{R_5} + \frac{V_{out}}{\frac{1}{sC_1}} = 0$$

$$\Rightarrow V_{out} - V_2 = -sC_1 R_5 V_{out}$$

Substitute  $V_2$ :


$$\Rightarrow (sC_1 R_5 + 1) V_{out} = V_2 = \frac{1}{0.01 s} (V_i - V_{out})$$

$$\Rightarrow (0.2s+1)(0.01s)V_{out} + V_{out} = V_i$$

$$\Rightarrow \left( \frac{1}{500}s^2 + \frac{1}{100}s + 1 \right) V_{out} = V_i$$

$$\Rightarrow V_{out} = \frac{1}{0.002s^2 + 0.01s + 1} V_i \quad \#$$

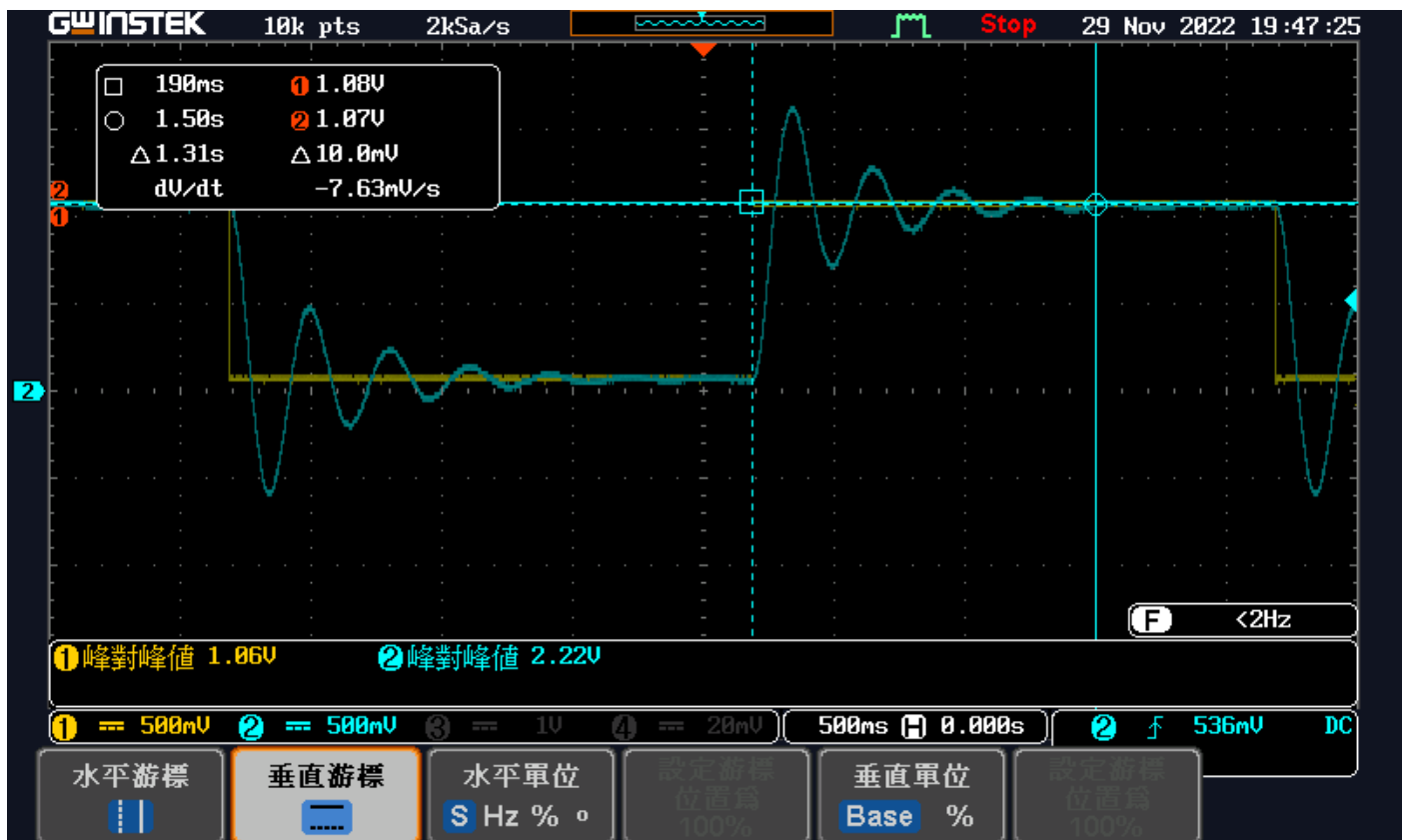2.  $V_{out}$  and  $V_{in}$  waveform (1 pic):




### 3. Simulation

Closed loop transfer function from command window:

$$\text{sys} = \frac{1}{0.002 s^2 + 0.01 s + 1}$$

The unit step response(1 pic):

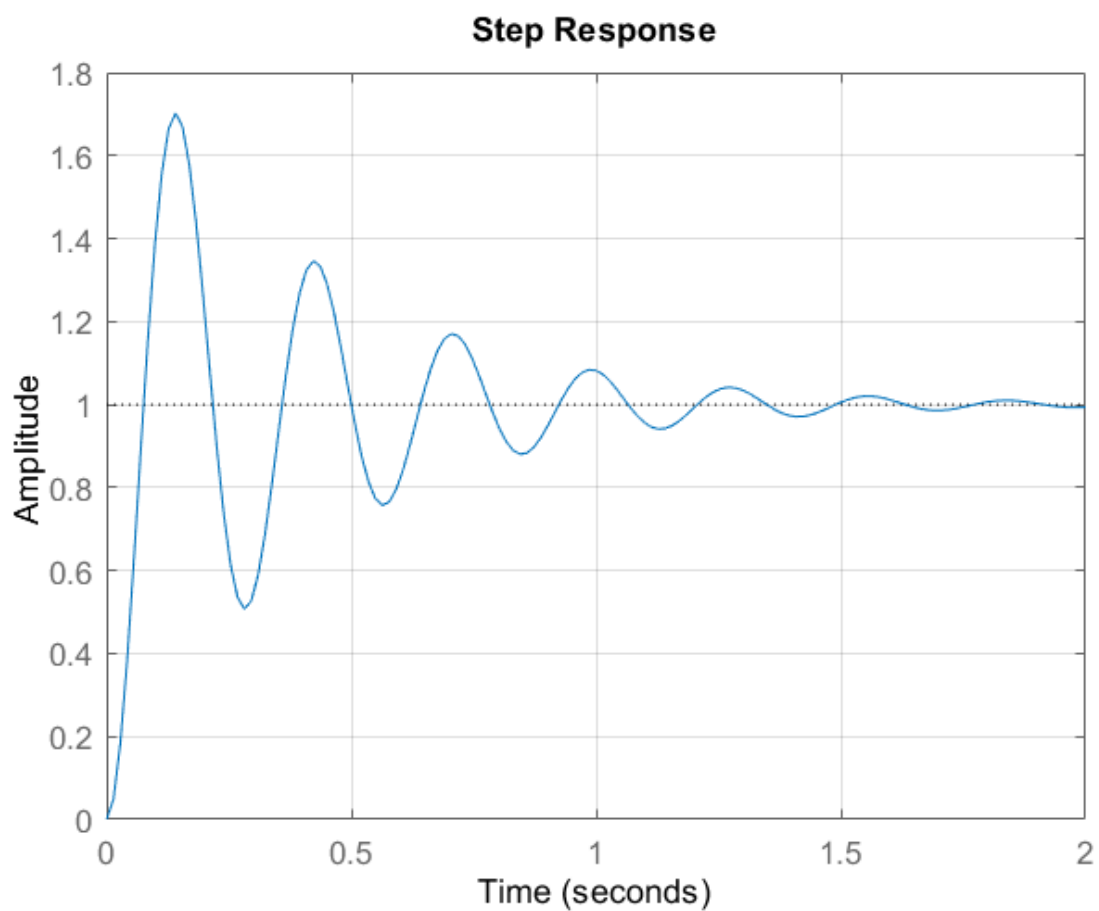

ans =

struct with fields:

```
RiseTime: 0.0509
SettlingTime: 1.5630
SettlingMin: 0.5072
SettlingMax: 1.7021
Overshoot: 70.2118
Undershoot: 0
```

Peak: 1.7021

PeakTime: 0.1405

delayTime =

0.2817

sserror =

0.0064

**Discuss:**


Try to explain why the steady-state error is close to zero and the effect of the gain  $K_I$  on the overall system.

When the output reach steady state, capacitor C2 will be open circuit because the current through it

$\frac{V_{out} - V_i - 0}{R_6}$  is approximately 0. Therefore, the steady state error is close to zero.

The effect of the gain  $K_I$  is to eliminate the steady state error.
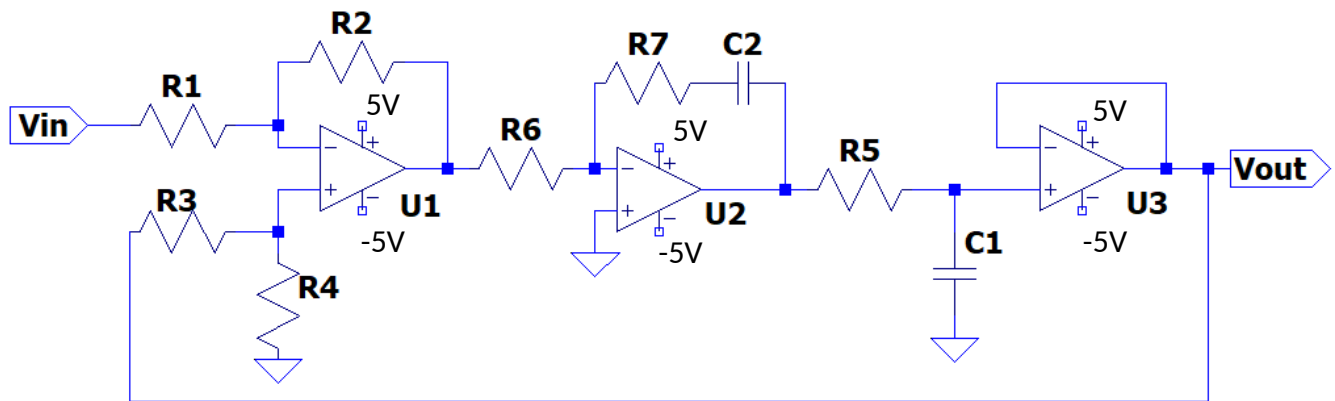
### Experiment 4: RC circuit with PI-controller and unit feedback



|                           | Maximum overshoot (%) | peak time (s) | rise time (s) | delay time (s) | settling time for 5% (s) | steady-state error (V) |
|---------------------------|-----------------------|---------------|---------------|----------------|--------------------------|------------------------|
| <b>Theoretical Result</b> |                       |               |               |                |                          | <b>0</b>               |
| <b>Experiment Result</b>  | <b>3.774</b>          | <b>0.085</b>  | <b>0.070</b>  | <b>0.019</b>   | <b>0.198</b>             | <b>0.004</b>           |
| <b>Simulation Result</b>  | <b>4.8838</b>         | <b>0.0974</b> | <b>0.0358</b> | <b>0.0127</b>  | <b>0.2007</b>            | <b>0.00064794</b>      |

注意事項:請參考投影片第7頁的定義

1. Calculate  $K_p$ ,  $K_I$  and the closed loop transfer function.

The difference amplifier:

$$V_1 = V_{out} - V_i$$

The PI controller:

$$\frac{0 - V_1}{R_6} + \frac{0 - V_2}{R_7 + \frac{1}{sC_2}} = 0$$

$$\Rightarrow \frac{V_2}{sC_2 R_7 + 1} = \frac{-V_1}{R_6}$$

$$\Rightarrow V_2 = \frac{-1}{R_6} \times \frac{sC_2 R_7 + 1}{sC_2} V_1$$

$$\dot{V}_1 - \frac{C_2 R_7 s + 1}{sC_2 R_6} V_1$$

$$\dot{V}_1 \frac{\frac{s}{10} + 1}{\frac{s}{100}} (V_i - V_{out})$$

$$\dot{V}_1 \frac{10s + 100}{s} (V_i - V_{out})$$

$$\Rightarrow \underline{K_p = 10, K_I = 100}_{\#}$$

The plant:

$$\frac{V_{out}}{sC_1} + \frac{V_{out} - V_2}{R_5} = 0$$

$$\Rightarrow (sC_1R_5 + 1)V_{out} = V_2$$

$$\Rightarrow V_{out} = \frac{1}{sC_1R_5 + 1} V_2$$


$$\hookrightarrow \frac{1}{0.2s + 1} \left( \frac{10s + 100}{s} \right) (V_i - V_{out})$$

$$\hookrightarrow \frac{10s + 100}{0.2s^2 + s} (V_i - V_{out})$$

$$\Rightarrow V_{out} = \frac{\frac{10s + 100}{0.2s^2 + s}}{1 + \frac{10s + 100}{0.2s^2 + s}} V_i$$

$$\Rightarrow V_{out} = \frac{10s + 100}{0.2s^2 + 11s + 100} V_i \quad \#$$

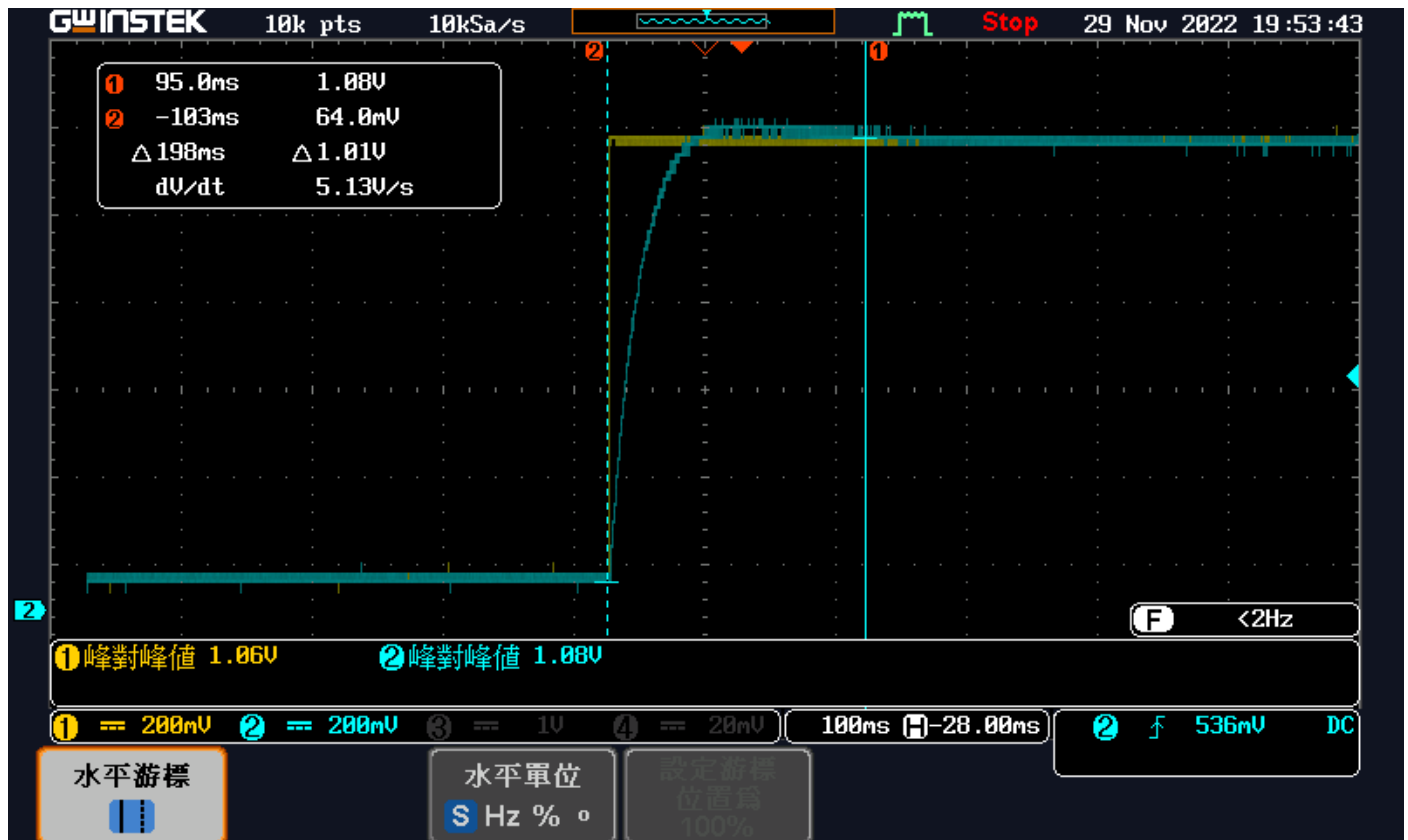2.  $V_{out}$  and  $V_{in}$  waveform (1 pic):




### 3. Simulation

Closed loop transfer function from command window:

sys =

$$\frac{0.1 s + 1}{0.002 s^2 + 0.11 s + 1}$$

The unit step response(1 pic):

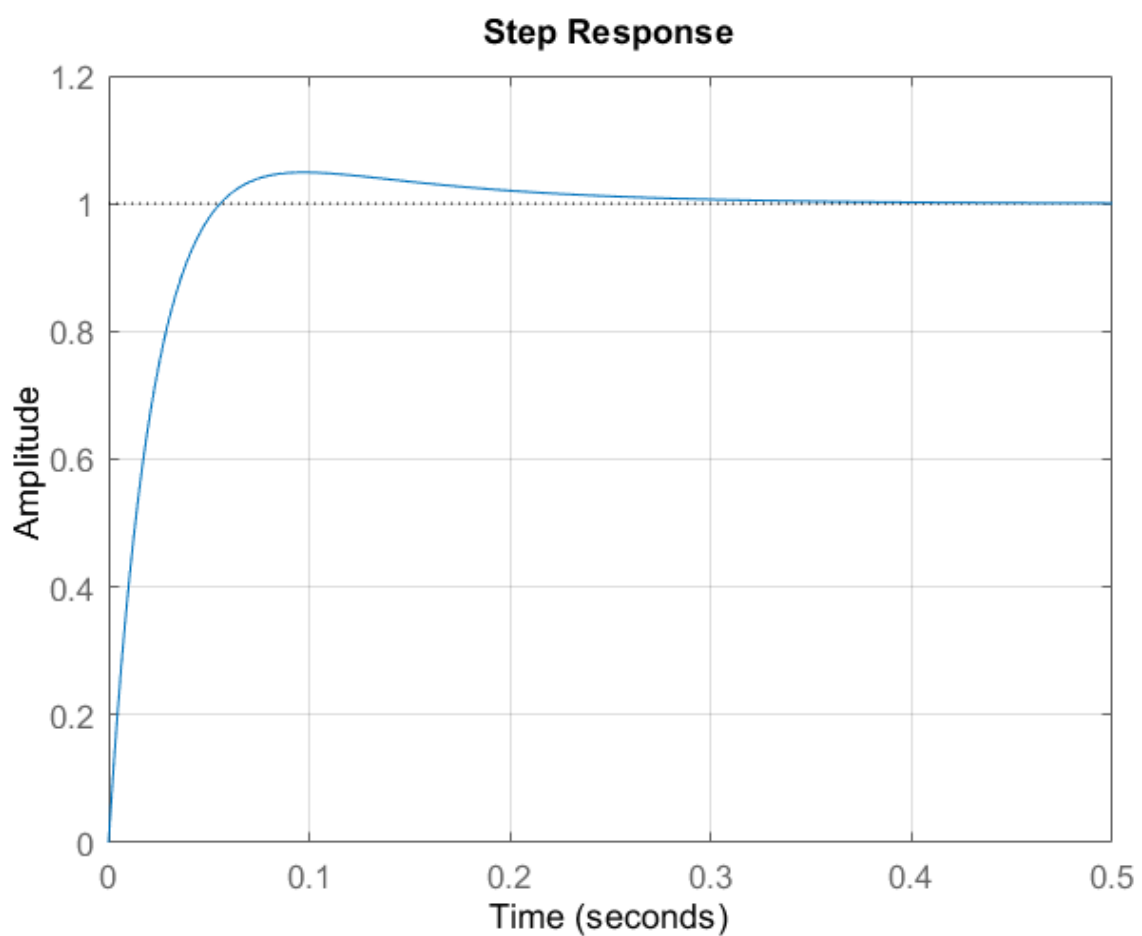

ans =

struct with fields:

```
RiseTime: 0.0358
SettlingTime: 0.2007
SettlingMin: 0.9017
SettlingMax: 1.0488
Overshoot: 4.8838
Undershoot: 0
```

Peak: 1.0488

PeakTime: 0.0974

delayTime =

0.0127

sserror =

6.4794e-04

**Discuss:**

Try to explain the effect of PI-controller on the overall system and how to design  $K_p$  and  $K_I$ .

The PI-controller both the rise time and the steady state errors of the system.

Increasing  $K_p$  results in a faster response of the control system. However, an increase in  $K_p$  above a certain value can make the system unstable.

Increasing  $K_i$  helps in eliminating steady-state error, but increases oscillations and overshoot.